

Down Counter: Synchronous

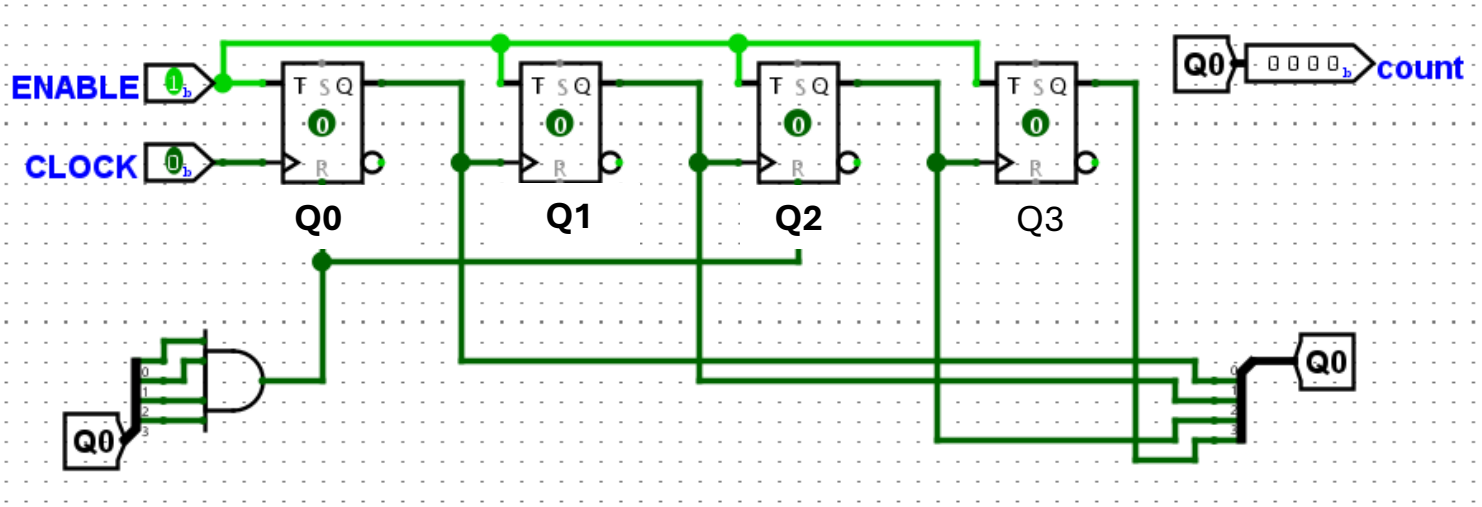

This doesn't Work, the reason it doesn't is because between 8 and 7 all inputs are 1, setting the Q0 and Q2 to 0, setting the number to 0010 (or 2 in decimal).


10 Count Down: Asynchronous

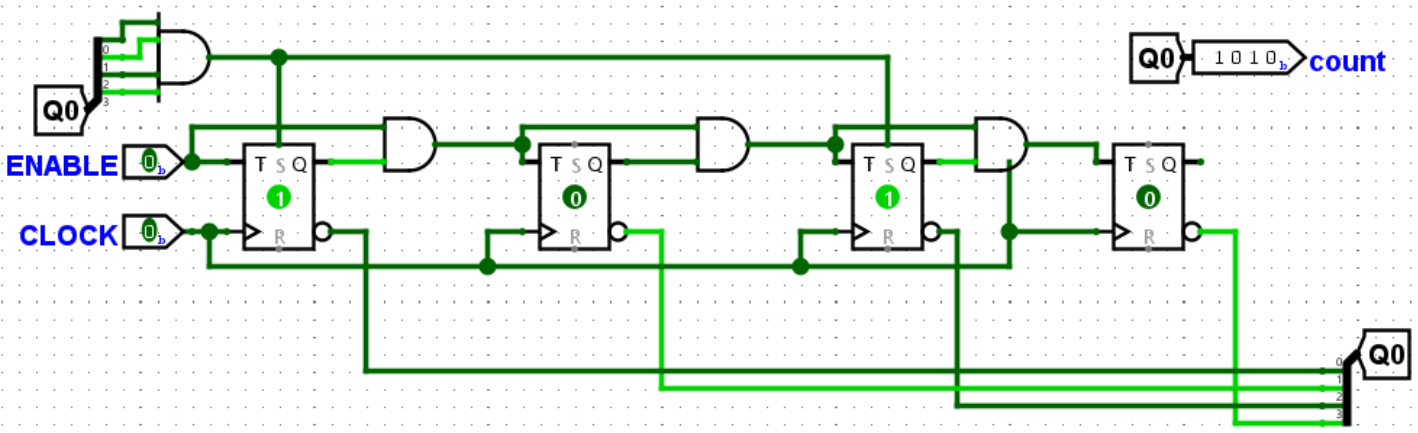

Counts down from Binary 1010 to 0000

Truth Table				
Q3	Q2	Q1	Q0	Decimal Count
1	0	1	0	10
1	0	0	1	9
1	0	0	0	8
0	1	1	1	7
0	1	1	0	6
0	1	0	1	5
0	1	0	0	4
0	0	1	1	3
0	0	1	0	2
0	0	0	1	1
0	0	0	0	0

Decimal Digital Display

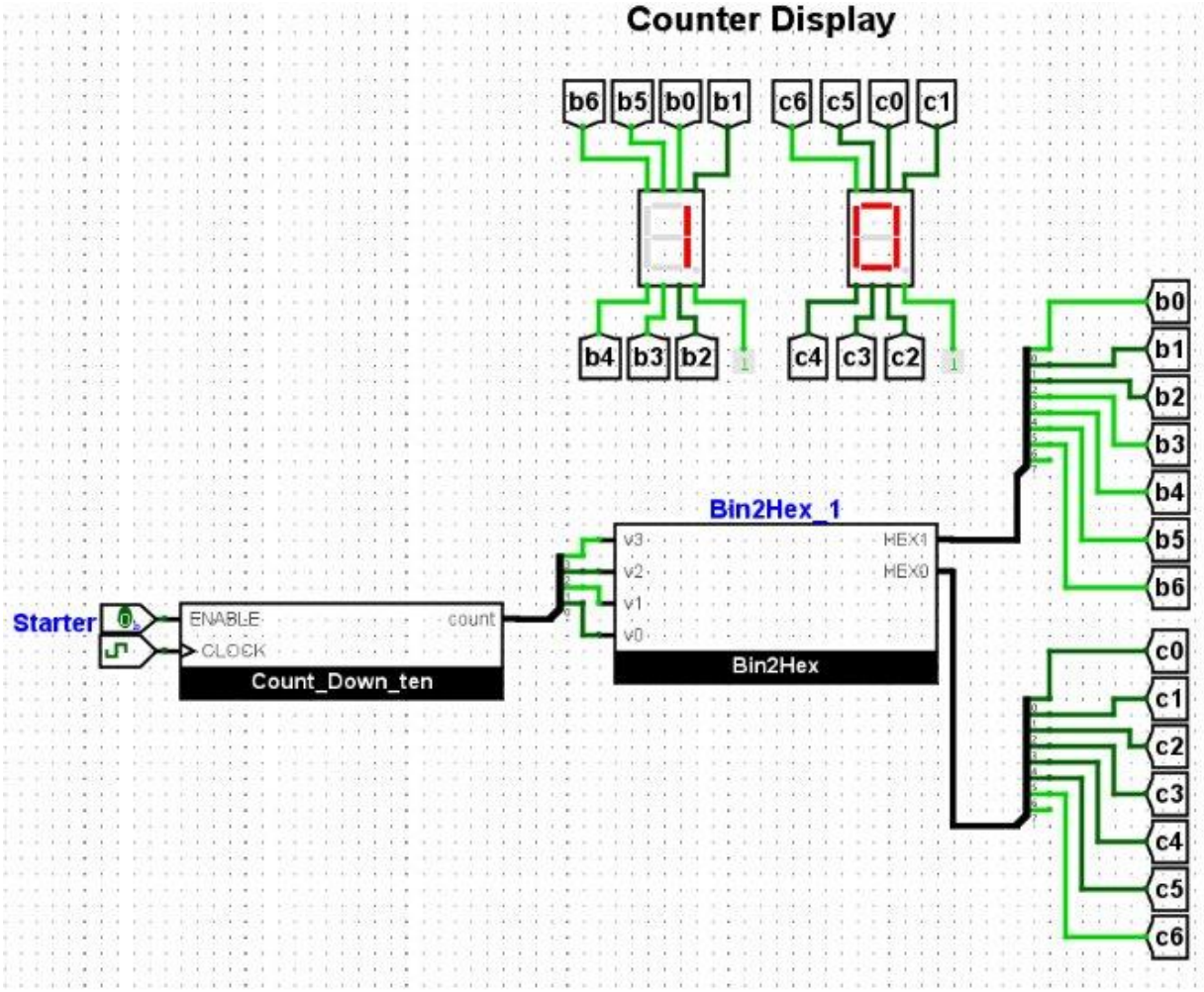

Displays the decimal value of the Count Down Circuit